

# DDCO LAB SEM3


Name : H M Mythreya

SRN : PES2UG20CS130

Section : C

Week 3: Adders


## Half Adder

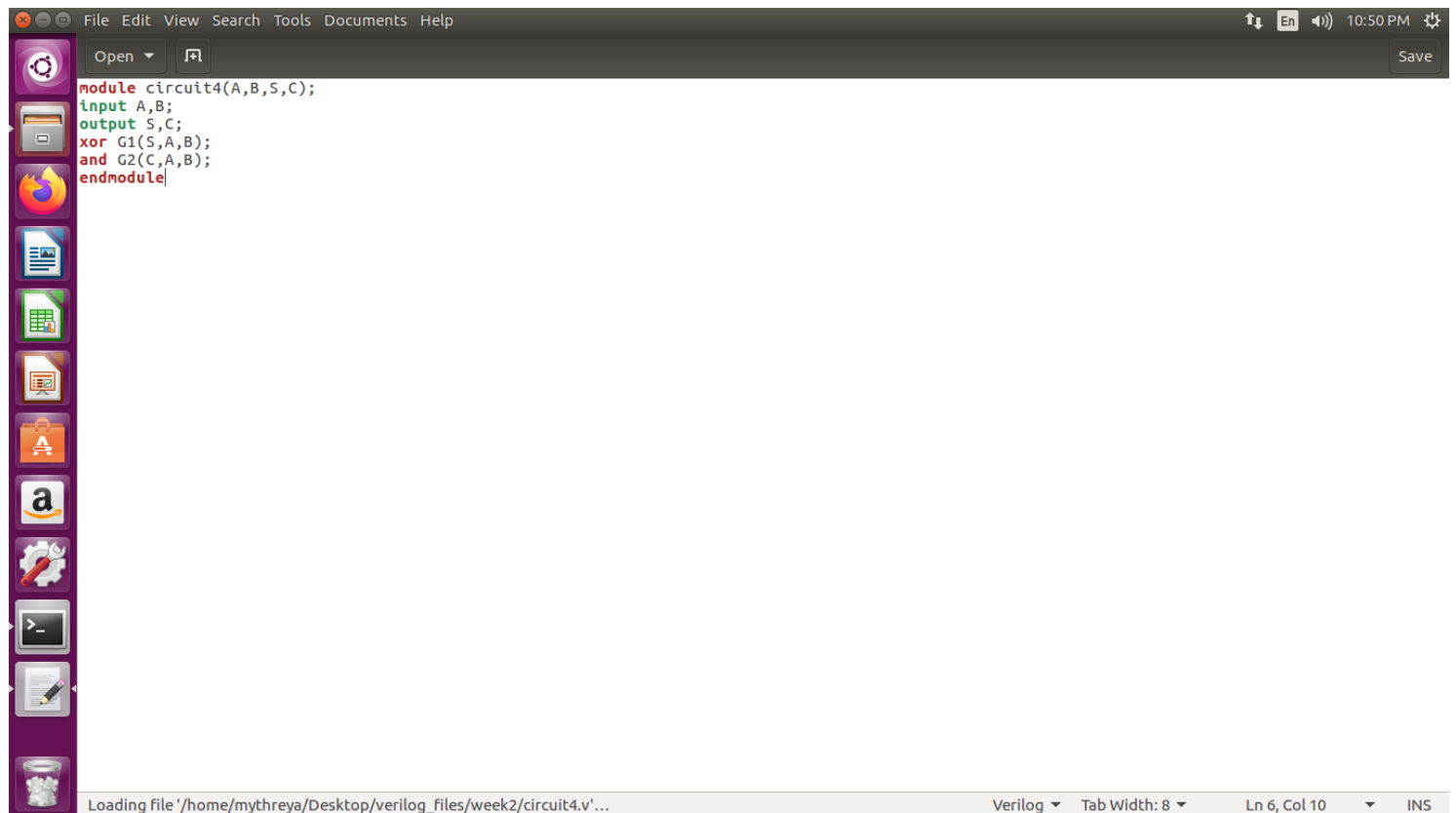

A screenshot of a Verilog code editor window. The title bar shows 'File Edit View Search Tools Documents Help' and system icons on the right. The code is as follows:

```
module circuit4(A,B,S,C);  
input A,B;  
output S,C;  
xor G1(S,A,B);  
and G2(C,A,B);  
endmodule
```

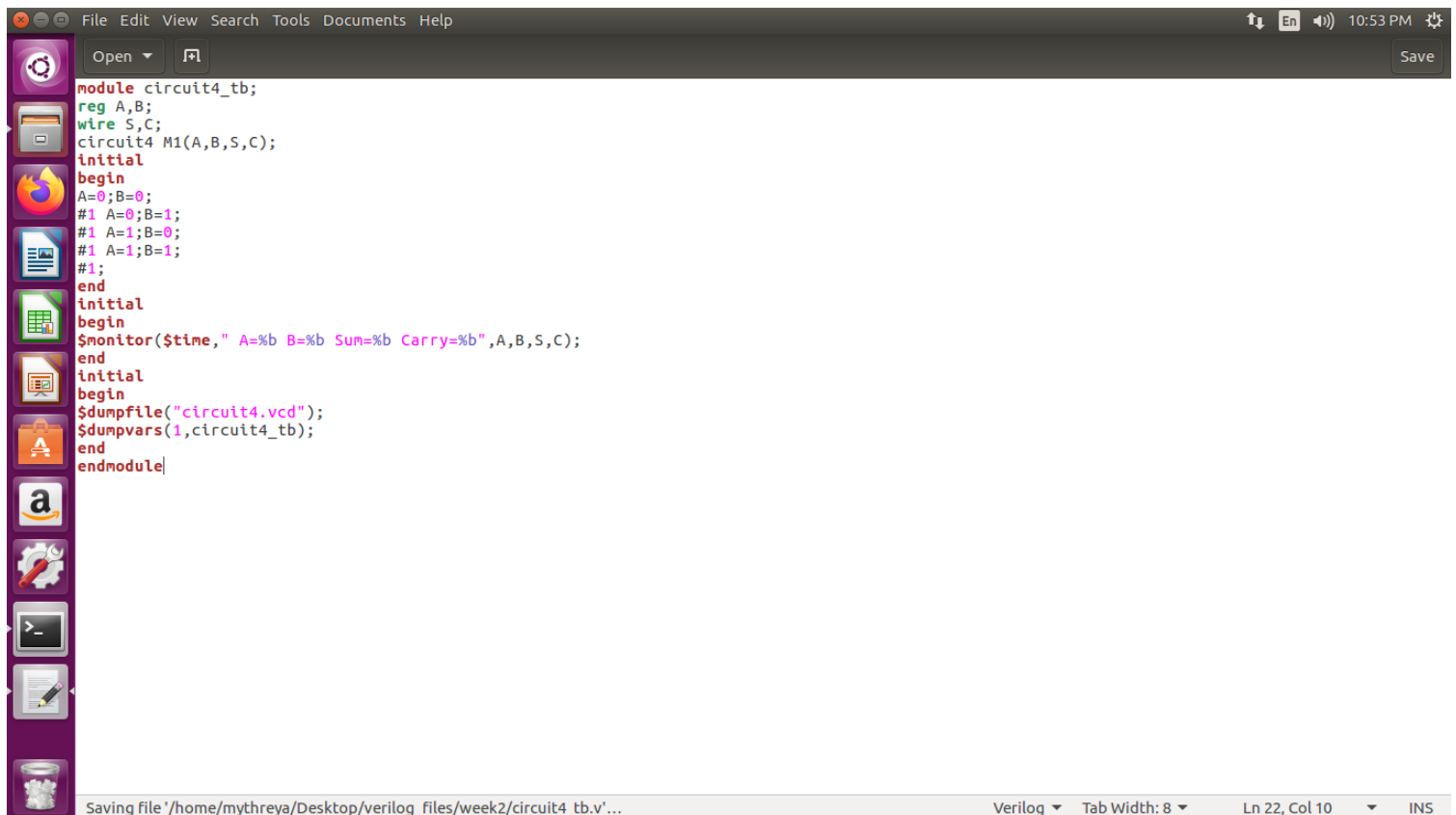The status bar at the bottom indicates 'Loading file "/home/mythreya/Desktop/verilog\_files/week2/circuit4.v'...', 'Verilog', 'Tab Width: 8', 'Ln 6, Col 10', and 'INS'.





A screenshot of a Verilog code editor window showing a testbench for the circuit4 module. The code is as follows:


```
module circuit4_tb;  
reg A,B;  
wire S,C;  
circuit4 M1(A,B,S,C);  
initial  
begin  
A=0;B=0;  
#1 A=0;B=1;  
#1 A=1;B=0;  
#1 A=1;B=1;  
#1;  
end  
initial  
begin  
$monitor($time," A=%b B=%b Sum=%b Carry=%b",A,B,S,C);  
end  
initial  
begin  
$dumpfile("circuit4.vcd");  
$dumpvars(1,circuit4_tb);  
end  
endmodule
```

The status bar at the bottom indicates 'Saving file "/home/mythreya/Desktop/verilog\_files/week2/circuit4\_tb.v'...', 'Verilog', 'Tab Width: 8', 'Ln 22, Col 10', and 'INS'.

# Output

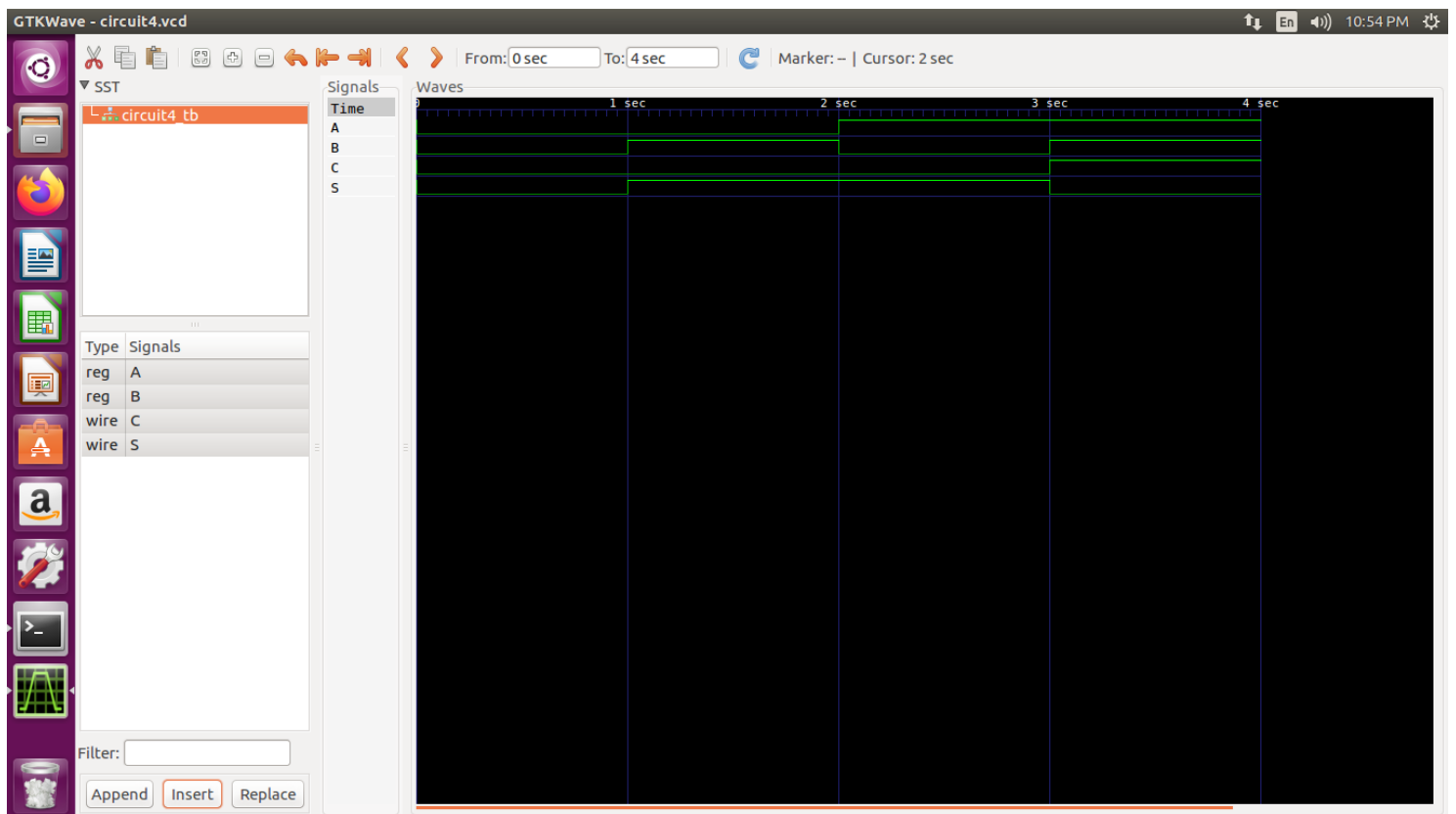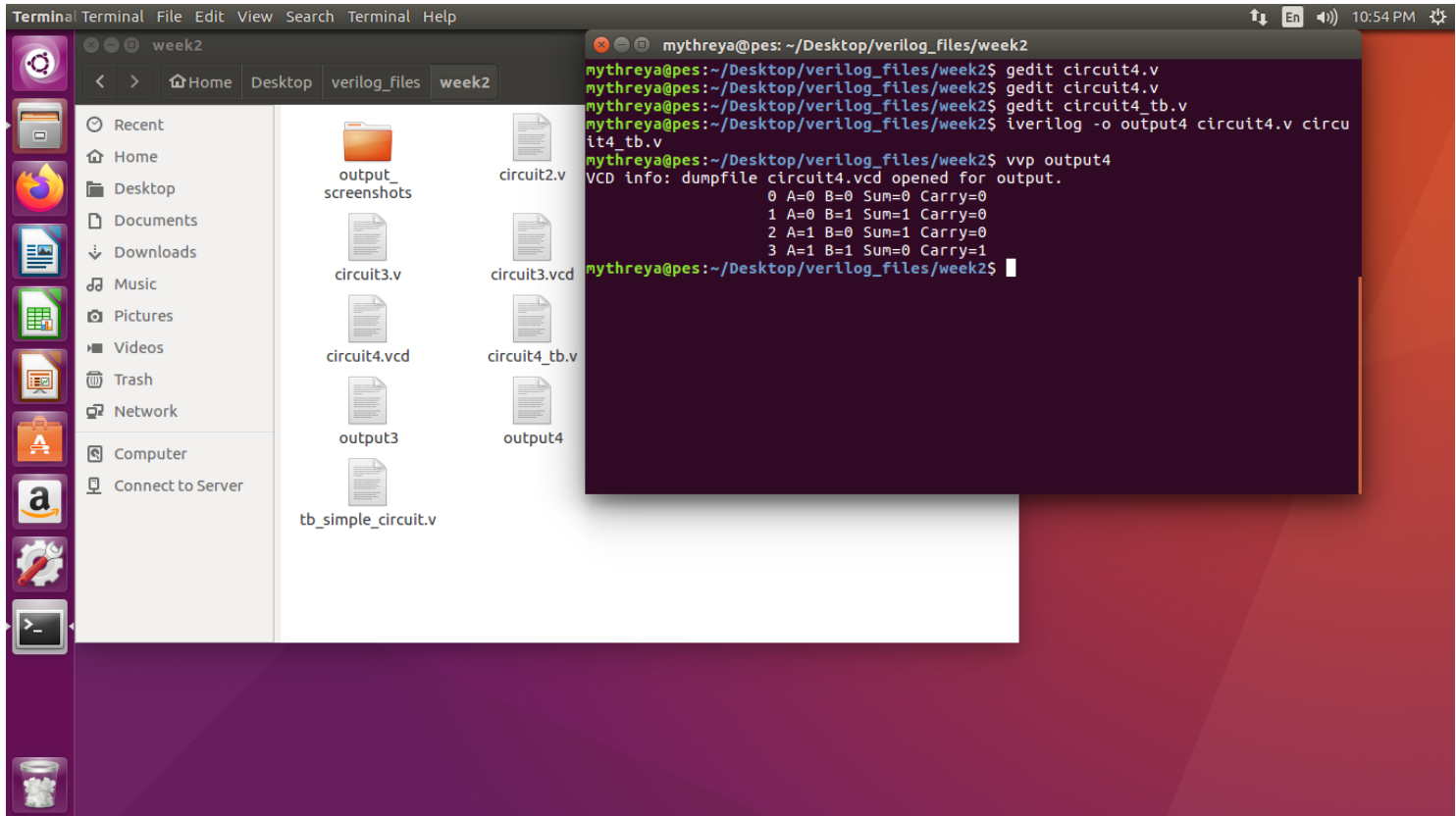


# Full Adder

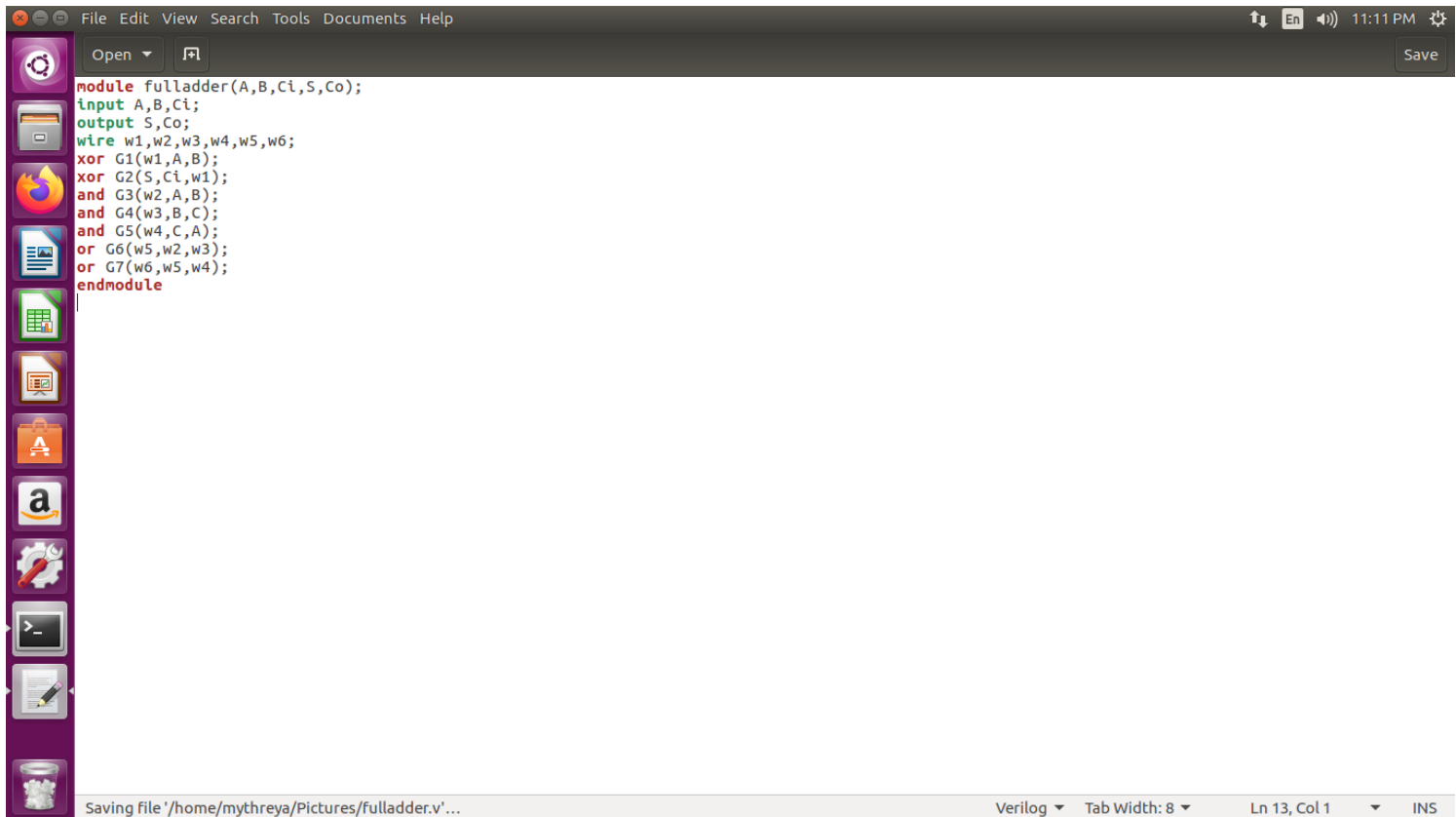

The screenshot shows a Verilog code editor window with a dark theme. The menu bar includes File, Edit, View, Search, Tools, Documents, and Help. The status bar at the bottom indicates the file is 'Verilog', tab width is 8, and the cursor is at line 13, column 1. The code defines a module named 'fulladder' with inputs A, B, Ci and outputs S, Co. It uses a series of XOR and AND gates to calculate the sum (S) and carry-out (Co) based on the inputs A, B, and the carry-in (Ci).

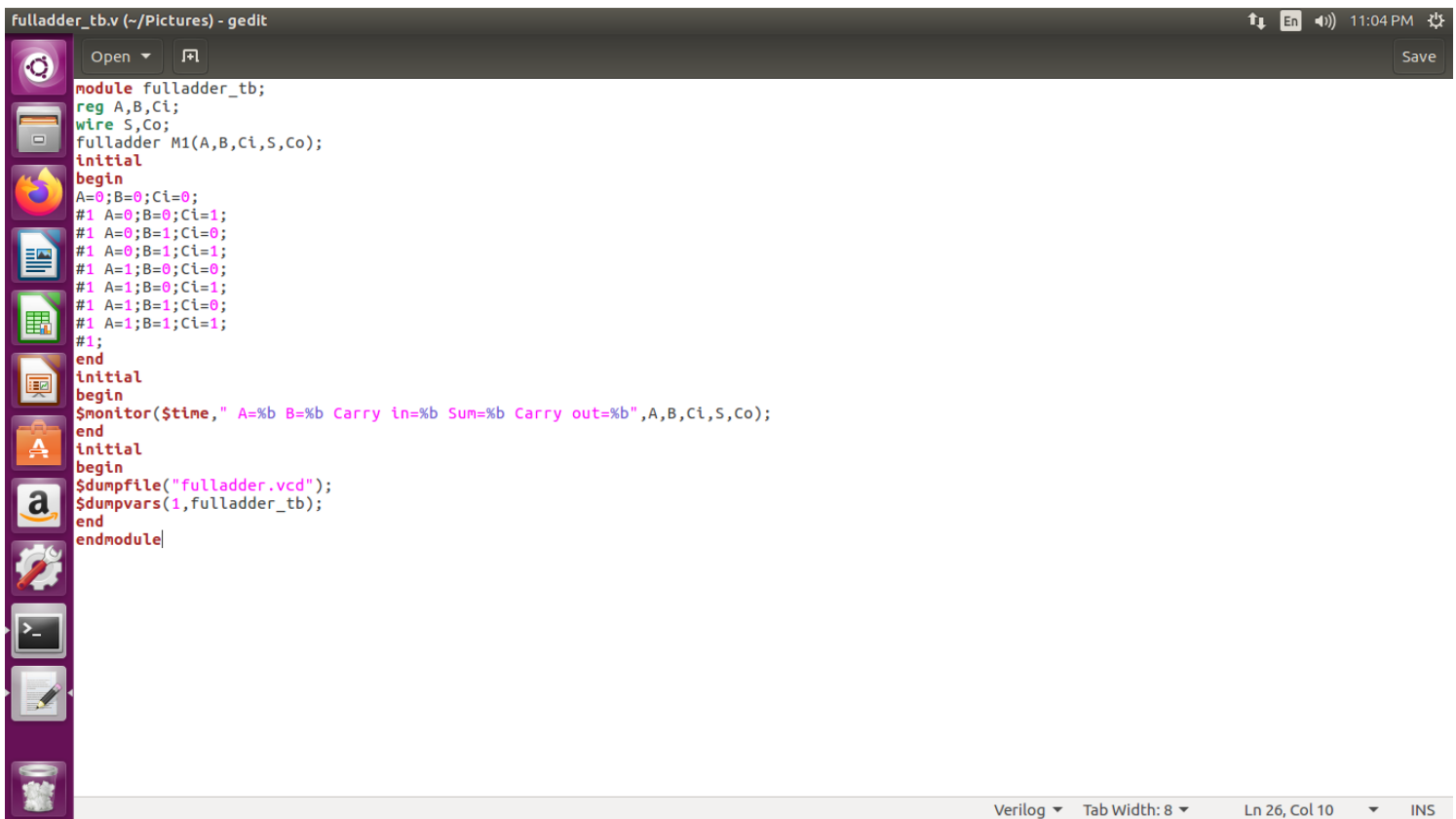
```
module fulladder(A,B,Ci,S,Co);
input A,B,Ci;
output S,Co;
wire w1,w2,w3,w4,w5,w6;
xor G1(w1,A,B);
xor G2(S,Ci,w1);
and G3(w2,A,B);
and G4(w3,B,C);
and G5(w4,C,A);
or G6(w5,w2,w3);
or G7(w6,w5,w4);
endmodule
```



The screenshot shows a Verilog testbench code editor window titled 'Fulladder\_tb.v (~/.Pictures) - gedit'. The status bar at the bottom indicates the file is 'Verilog', tab width is 8, and the cursor is at line 26, column 10. The testbench module 'fulladder\_tb' instantiates the 'fulladder' module and applies a series of test cases for inputs A, B, and Ci. It uses a \$monitor system task to display the results of the sum (S) and carry-out (Co) for each test case, and a \$dumpfile system task to save the simulation results to a VCD file.


```
module fulladder_tb;
reg A,B,Ci;
wire S,Co;
fulladder M1(A,B,Ci,S,Co);
initial
begin
A=0;B=0;Ci=0;
#1 A=0;B=0;Ci=1;
#1 A=0;B=1;Ci=0;
#1 A=0;B=1;Ci=1;
#1 A=1;B=0;Ci=0;
#1 A=1;B=0;Ci=1;
#1 A=1;B=1;Ci=0;
#1 A=1;B=1;Ci=1;
#1;
end
initial
begin
$monitor($time," A=%b B=%b Carry in=%b Sum=%b Carry out=%b",A,B,Ci,S,Co);
end
initial
begin
$dumpfile("fulladder.vcd");
$dumpvars(1,fulladder_tb);
end
endmodule
```

# Output

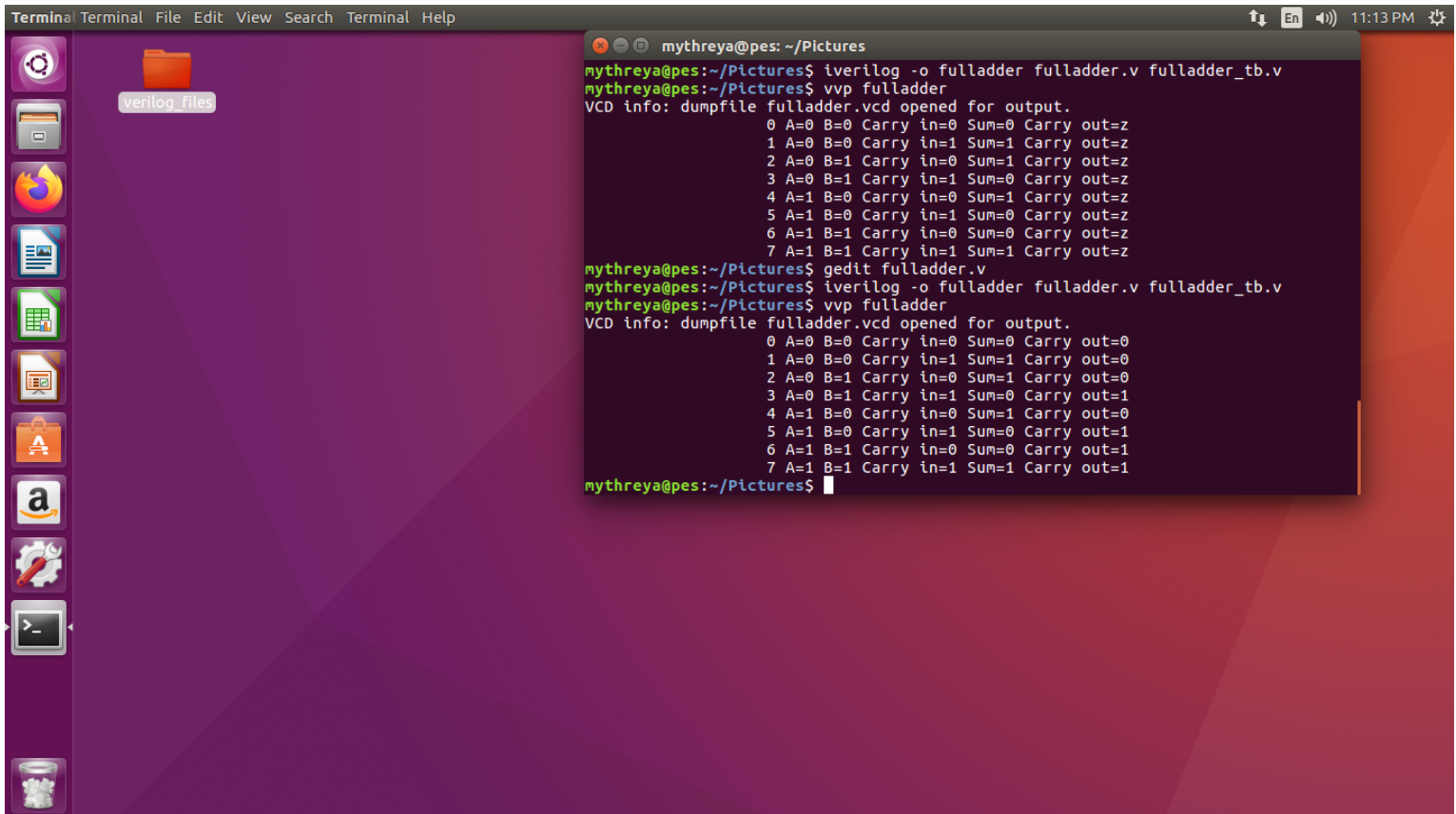

The screenshot shows a Linux desktop with a purple background. A terminal window is open, displaying the following commands and output:

```
mythreya@pes: ~/Pictures
mythreya@pes:~/Pictures$ iverilog -o fulladder fulladder.v fulladder_tb.v
mythreya@pes:~/Pictures$ vvp fulladder
VCD info: dumpfile fulladder.vcd opened for output.
 0 A=0 B=0 Carry in=0 Sum=0 Carry out=z
 1 A=0 B=0 Carry in=1 Sum=1 Carry out=z
 2 A=0 B=1 Carry in=0 Sum=1 Carry out=z
 3 A=0 B=1 Carry in=1 Sum=0 Carry out=z
 4 A=1 B=0 Carry in=0 Sum=1 Carry out=z
 5 A=1 B=0 Carry in=1 Sum=0 Carry out=z
 6 A=1 B=1 Carry in=0 Sum=0 Carry out=z
 7 A=1 B=1 Carry in=1 Sum=1 Carry out=z
mythreya@pes:~/Pictures$ gedit fulladder.v
mythreya@pes:~/Pictures$ iverilog -o fulladder fulladder.v fulladder_tb.v
mythreya@pes:~/Pictures$ vvp fulladder
VCD info: dumpfile fulladder.vcd opened for output.
 0 A=0 B=0 Carry in=0 Sum=0 Carry out=0
 1 A=0 B=0 Carry in=1 Sum=1 Carry out=0
 2 A=0 B=1 Carry in=0 Sum=1 Carry out=0
 3 A=0 B=1 Carry in=1 Sum=0 Carry out=1
 4 A=1 B=0 Carry in=0 Sum=1 Carry out=0
 5 A=1 B=0 Carry in=1 Sum=0 Carry out=1
 6 A=1 B=1 Carry in=0 Sum=0 Carry out=1
 7 A=1 B=1 Carry in=1 Sum=1 Carry out=1
mythreya@pes:~/Pictures$
```

 


## Ripple Carry Adder (rca)

```
module rca(input wire[3:0] a,b,input wire cin,output wire[3:0] sum,output wire cout);
output wire[2:0] c;
fulladder u0(a[0],b[0],cin,sum[0],c[0]);
fulladder u1(a[1],b[1],c[0],sum[1],c[1]);
fulladder u2(a[2],b[2],c[1],sum[2],c[2]);
fulladder u3(a[3],b[3],c[2],sum[3],cout);
endmodule
```

```
`timescale 1 ns / 100 ps
`define TESTVECS 10
module tb;
reg clk, reset;
reg [3:0] i0, i1;
reg cin;
wire [3:0] o;
wire cout;
reg [8:0] test_vecs [0:(`TESTVECS-1)];
integer i;
initial begin
$dumpfile("rca_test.vcd");
$dumppvars(0,tb);
end
initial begin
reset = 1'b1; #12.5 reset = 1'b0; end
initial clk = 1'b0; always #5 clk =~ clk;
initial begin
test_vecs[0] = 9'b000000000;
test_vecs[1] = 9'b000000001;
test_vecs[2] = 9'b000100010;
test_vecs[3] = 9'b000100011;
test_vecs[4] = 9'b001000100;
test_vecs[5] = 9'b101010110;
test_vecs[6] = 9'b101010111;
test_vecs[7] = 9'b110011010;
test_vecs[8] = 9'b111111100;
test_vecs[9] = 9'b111111101;
end
initial {i0, i1, cin, i} = 0;
rca u0 (i0, i1, cin, o, cout);
initial begin
#6 for(i=0;i<`TESTVECS;i=i+1)
|   begin #10 {i0, i1, cin}=test_vecs[i]; end
#100 $finish;
end
always@(i0 or i1 or cin)
$monitor("At time = %t, i0=%b, i1=%b,cin=%b,Sum = %b,Carry %b", $time,i0,i1,cin,o,cout);
endmodule
```
 
# Output

```
PS X:\sem3\sem3-lab\ddco_lab\week3\rippleCarryAdder> vvp rca
VCD info: dumpfile rca_test.vcd opened for output.
At time =          0, i0=0000, i1=0000,cin=0,Sum = 00x0,Carry 0
At time =        260, i0=0000, i1=0000,cin=1,Sum = 00xx,Carry 0
At time =        360, i0=0001, i1=0001,cin=0,Sum = 00xx,Carry 0
At time =        460, i0=0001, i1=0001,cin=1,Sum = 00x1,Carry 0
At time =        560, i0=0010, i1=0010,cin=0,Sum = 01x0,Carry 0
At time =        660, i0=1010, i1=1011,cin=0,Sum = 01x1,Carry 1
At time =        760, i0=1010, i1=1011,cin=1,Sum = 01xx,Carry 1
At time =        860, i0=1100, i1=1101,cin=0,Sum = 10xx,Carry 1
At time =        960, i0=1111, i1=1110,cin=0,Sum = 11xx,Carry 1
At time =       1060, i0=1111, i1=1110,cin=1,Sum = 11xx,Carry 1
rca tb.v:60: $finish called at 2060 (100ps)
```



Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature:

Name:

SRN:

Section:

Date: